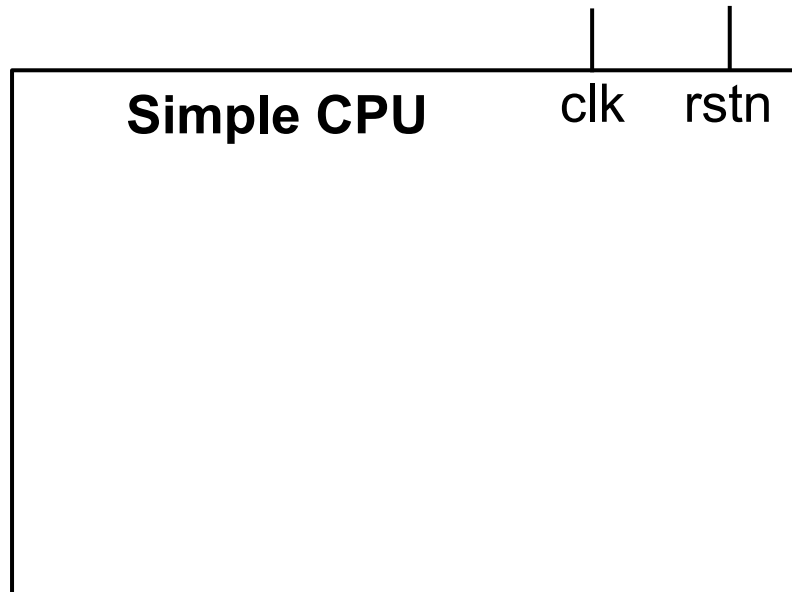


You should add wires to this diagram to complete the project

Ports



- Input
 - clk : clock input
 - rstn : for resetting the cpu

Ports




- Input
 - PC (32b) : address of instruction
- Output
 - instruction (32b) : instruction for current PC

Ports



- Input
 - instruction (32b): instruction
- Output
 - sextimm (32b): sign-extended immediate

Ports

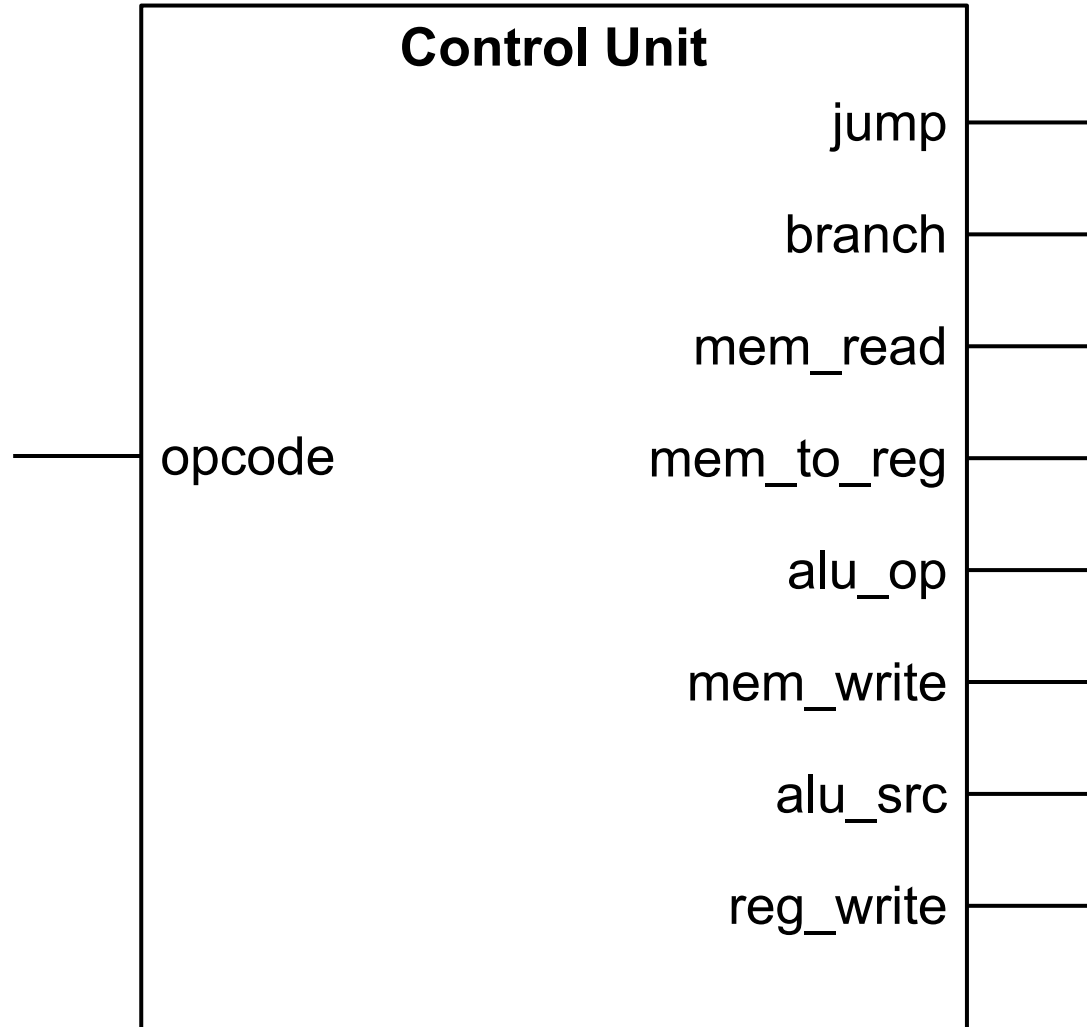


- **Input**

- opcode (7b) : opcode from instruction

- **Output**

- jump (2b) : indicates if this inst is “jal” or “jalr”
- branch (1b) : indicates if this inst is a branch type
- mem_read (1b) : indicates whether to read from memory
- mem_to_reg (1b)
 - 0 : writeback source is from ALU
 - 1 : writeback source is from memory
- alu_op (2b) : control signal sent to ALU control
- mem_write (1b) : indicates whether to write to memory
- alu_src (1b)
 - 0 : in_b of ALU is from the register file
 - 1 : in_b of ALU is from the immediate generator
- reg_write (1b) : indicates whether to perform writeback to the register file

Ports

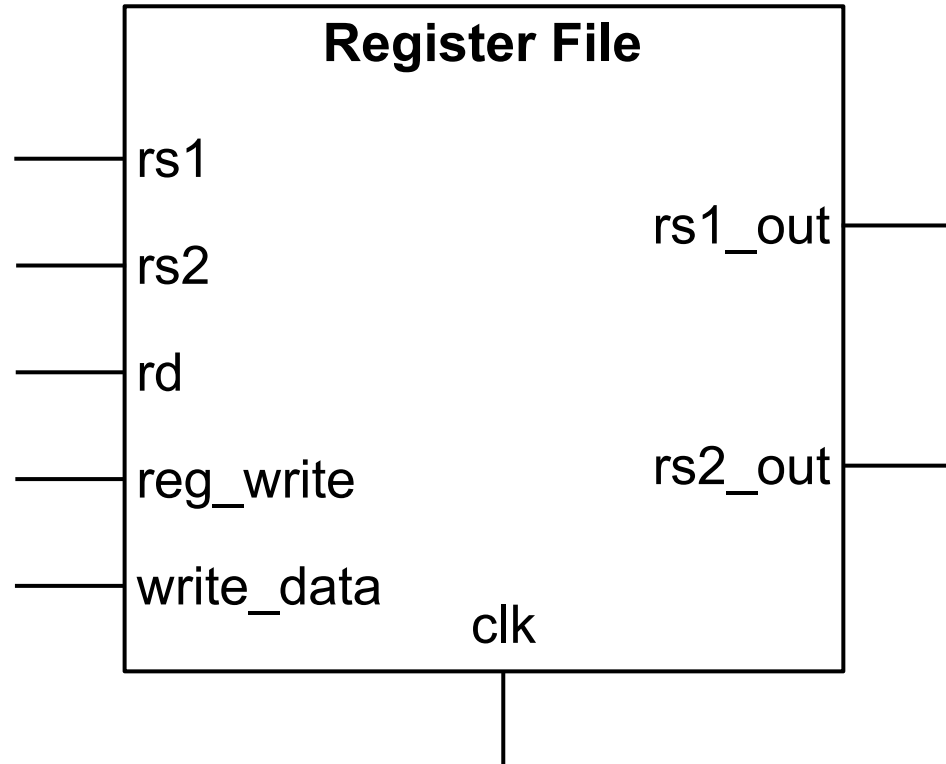


- Input

- rs1 (5b) : source 1 register file index
- rs2 (5b) : source 2 register file index
- rd (5b) : destination register file index
- reg_write (1b)
 - 0 : do not write write_data to register file
 - 1 : update rd with write_data
- write_data (32b) : data which will be written to the register file

- Output


- rs1_out (32b) : data from rs1
- rs2_out (32b) : data from rs2

Ports

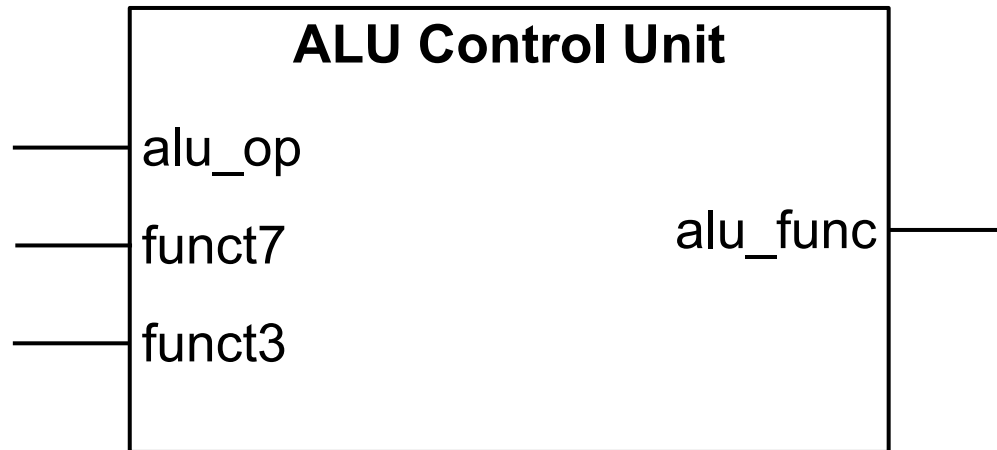


- Input
 - alu_op (2b) : from control unit
 - ▶ 00 : select operation for loads/stores
 - ▶ 01 : select operation for branches
 - ▶ 10 : select operation for R types
 - ▶ 11 : select operation for I types
 - funct7 (7b) : from instruction
 - funct3 (3b) : from instruction
- Output
 - alu_func (4b) : ALU operation control signals

Ports

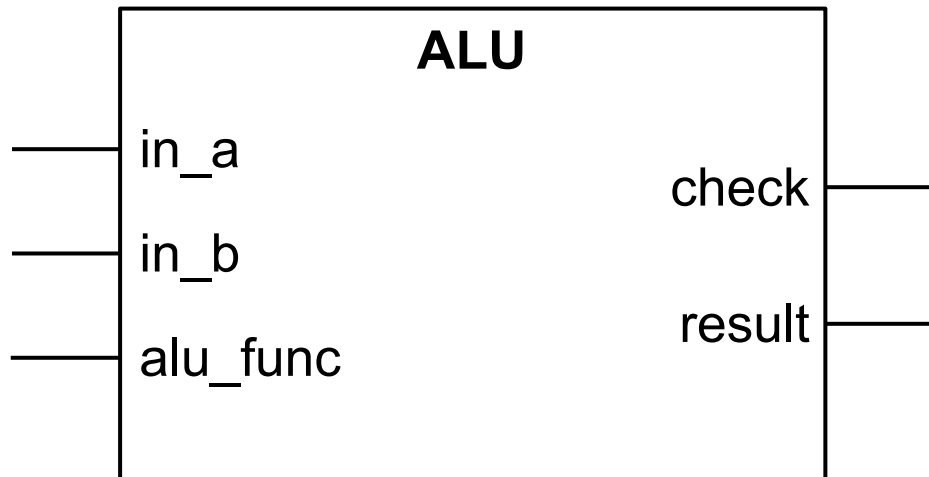


- Input
 - in_a (32b) : ALU source operand
 - in_b (32b) : ALU source operand
 - alu_func (4b) : specifies which operation the ALU should execute
- Output
 - result (32b) : ALU operation result
 - check (1b) : check flag for branches

Ports

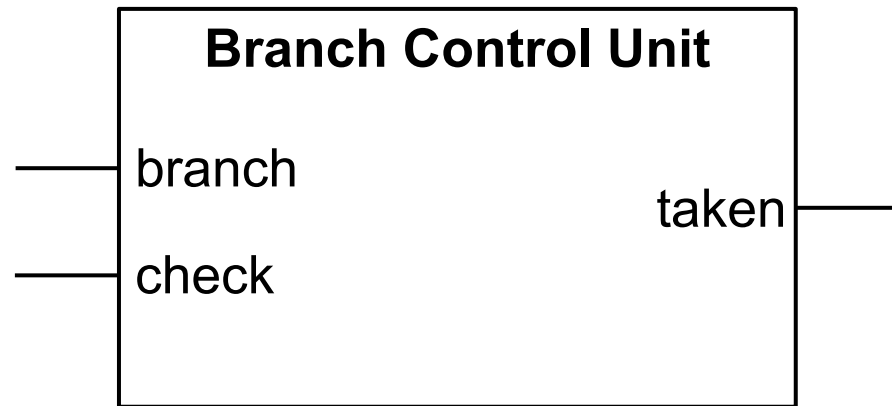

- Input
 - branch (1b) : instruction is a branch type or not
 - check (1b) : output from ALU
- Output
 - taken (1b) : set to 1 if branch is taken

Ports

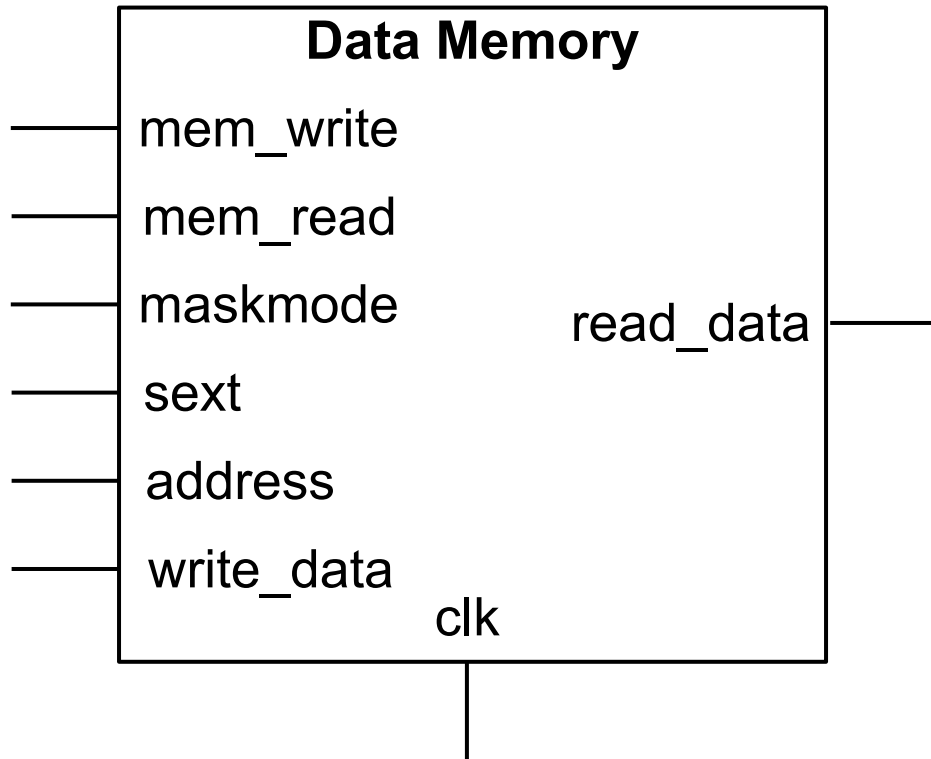

- Input
 - address (32b) : memory address
 - write_data (32b) : data which will be written
 - mem_read (1b) : indicates whether to read from memory
 - mem_write (1b) : indicates whether to write to memory
 - maskmode (2b)
 - 0 : byte
 - 1 : half-word
 - 2 : word
 - sext (1b)
 - 0 : output read_data as sign extend
 - 1 : output read_data as unsigned (zero extend)
- Output
 - read_data (32b) : data read from the memory